



SREE CHITRA TIRUNAL INSTITUTE FOR MEDICAL SCIENCES & TECHNOLOGY  
THIRUVANANTHAPURAM—695 011, INDIA.

(An Institute of National Importance under Govt.of India)

Phone—(91)0471—2443152 Fax—(91)0471—2446433, 2550728

Email-sct@sctimst.ac.in Web site—www.sctimst.ac.in

ROLL NUMBER

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS) – A

DATE : 07/07/2017

TIME : 09.30 AM

DURATION : 60 MINUTES

TOTAL MARKS : 60


INSTRUCTIONS TO THE CANDIDATE

1. Write your Roll Number on the top of the Question Booklet and in the OMR sheet.
2. Each question carries 1 mark.
3. There will not be any Negative Marking.
4. Darken only the bubble corresponding to the most appropriate answer.
5. Marking more than one answer will invalidate the answer.
6. Candidate should sign on the question paper and OMR sheet.
7. Candidate should hand over the question paper and OMR sheet to the invigilator before leaving the examination hall.

Signature of the Candidate

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

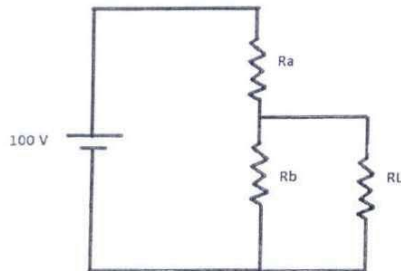1. Which of the following has the ability to act as open circuit for DC and a short circuit for AC of high frequency?  
(A) An inductor (B) A capacitor  
(C) A resistor (D) None of the above
2. What is the voltage across the load resistance  $R_L$  in the circuit below? The value of resistors connected in the circuit is  $R_a=R_b=R_L=100\Omega$   
(A) 3.33V (B) 33.33V  
(C) 333.33V (D) 66.6V



3. Materials not having negative temperature coefficient of resistance are  
(A) Metals (B) Semiconductors  
(C) Insulators (D) None of the above
4. Which of the following is a trivalent material?  
(A) Antimony (B) Phosphorus  
(C) Arsenic (D) Boron
5. LED's for their display require  
(A) A voltage of 1.2V and a current of 100mA (B) A voltage of 25V and a current of 100mA  
(C) A voltage of 1.2V and a current of 20mA (D) A voltage of 25V and a current of 20mA
6. A diode in which one can change the reverse bias and thus vary the capacitance is?  
(A) Zener diode (B) Tunnel diode  
(C) Varactor diode (D) Switching diode
7. A bipolar junction transistor with forward current transfer ratio  $\alpha=0.98$  when working in CE mode provides  $\beta$  as  
(A) 0.02 (B) 49  
(C) 0.49 (D) 98

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

8. In a JFET drain current is maximum when  $V_{GS}$  is  
(A) Zero (B) Negative  
(C) Positive (D) Equal to  $V_P$
9. A signal may have frequency components in the range of 0.001Hz to 10Hz. Which one of the following type of couplings should be chosen in a multistage amplifier designed to amplify the signal  
(A) RC coupling (B) Transformer coupling  
(C) Direct coupling (D) Double tuned transformer coupling
10. In a class A amplifier, conduction extends over  $360^\circ$  because the Q point is:  
(A) Located on load line (B) Located at or near cut-off point  
(C) Located near saturation (D) Centered on load line
11. If the Q of a single stage, single tuned amplifier is doubled then its bandwidth will  
(A) Remain same (B) Become half  
(C) Become double (D) Become four times
12. A differential amplifier is invariably used in the input stage of all op-amps. This is done to provide op-amps with very high  
(A) Open loop gain (B) Slew rate  
(C) Bandwidth (D) CMRR
13. A Hartley oscillator is used for generation of  
(A) Very low frequency (B) Radio frequency oscillation  
(C) Microwave oscillation (D) Audio frequency oscillation
14. In three RC combination of a RC phase shift oscillator each RC gives a phase shift of  
(A)  $45^\circ$  (B)  $90^\circ$   
(C)  $60^\circ$  (D)  $30^\circ$
15. In a centre tap full wave rectifier, 100 V is the peak voltage between the centre tap and one of the secondary. What is the maximum voltage across the reverse biased diode?  
(A) 200V (B) 141V  
(C) 100V (D) 186V
16. The primary function of a filter is to:  
(A) Minimize AC input variations (B) Suppress odd harmonics in the rectified output  
(C) Stabilize DC level of the output voltage (D) Remove ripples from the rectified output.

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

17. A mono-stable multi-vibrator  
(A) Has both the states as stable states  
(B) Makes transition from one state to another when trigger is applied  
(C) Has both the states as unstable states  
(D) Has one stable state and one quasi-stable state
18. The purpose of schmitt trigger circuit is to generate a  
(A) Triangular wave (B) Square wave  
(C) Sinusoidal wave (D) Sawtooth wave
19. An operational amplifier is basically a  
(A) Low gain AC amplifier (B) High gain RC coupled amplifier  
(C) High gain DC amplifier (D) High gain transformer coupled amplifier
20. For an op-amp  $CMRR=10^5$  and differential gain =  $10^5$ . What is the common mode gain of the op-amp?  
(A) 1 (B)  $2 \times 10^5$   
(C)  $10^{10}$  (D)  $10^5$
21. For ideal op-amp non-inverting amplifier with resistors  $R_1=2k\Omega$  and  $R_f=2k\Omega$ , the overall voltage gain can be  
(A) -2 (B) +1  
(C) +2 (D) +3
22. The voltage gain of an ideal voltage follower is  
(A) 1 (B)  $<1$   
(C) 0 (D) Infinity
23. An instrumentation amplifier uses  
(A) 1 op-amp (B) 2 op-amps  
(C) 4 op-amps (D) 3 op-amps
24. An SCR remains turned on if the anode current is more than  
(A) Breakover current (B) Holding current  
(C) Trigger current (D) Threshold current
25. Which of the following is used as the main switching element in a switched mode power supply operating in 20 kHz to 100kHz range  
(A) Thyristor (B) Triac  
(C) MOSFET (D) UJT

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

26. Which of the following controls reduces the size of transformer in a switched mode power supply?  
(A) Resonant circuit                      (B) Phase control  
(C) PWM control                          (D) Bidirectional control
27. Which of the following is a voltage regulator IC?  
(A) IC 555                                  (B) IC 7400  
(C) IC 844                                  (D) IC 723
28. When a Boolean expression contains 4 variables, the number of cells in the karnaugh map must be?  
(A)  $2^4$                                       (B)  $2^4-1$   
(C)  $2^3$                                       (D)  $2^4+1$
29. To form a half adder, which two gate combinations are essential?  
(A) AND & OR                              (B) AND & NOR  
(C) AND & NOT                              (D) AND & XOR
30. Binary 1011001 is equal to  
(A) 89 decimal                              (B) 100 decimal  
(C) 900 decimal                              (D) None of the above
31. The number of flip-flops required in a decade counter is  
(A) 2    (B) 3  
(C) 4    (D) 10
32. The logic family which has minimum power dissipation is  
(A) TTL                                      (B) I<sup>2</sup>L  
(C) ECL                                      (D) CMOS
33. Tunneling occurs in the tunnel diode  
(A) Only in the reverse direction              (B) Only when the forward voltage is high  
(C) When the bias is zero                      (D) In the forward direction at a very low voltage
34. Effect of reverse bias on a P-N junction is to:  
(A) Attract holes and electrons towards the junction  
(B) Increase the junction capacitance  
(C) Have no significant effect on the holes and electrons  
(D) Pulls holes and electrons away from the junctions
35. A current transformer  
(A) Should have its secondary open while primary is carrying current  
(B) Should never have its secondary open while the primary is carrying current

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

- (C) Is never used with the secondary circuit closed through ammeters, wattmeters, current coils or relay coils  
(D) None of the above
36. As per BIS, the number of accuracy classes of an instrument is:  
(A) 5 (B) 6  
(C) 7 (D) 8
37. LVDT  
(A) Converts linear motion into electrical signal  
(B) Translates electrical signal into linear motion  
(C) Helps measuring temperature  
(D) Can be used to sense angular displacement
38. The basic principle of LASER is  
(A) Stimulated absorption (B) Stimulated emission  
(C) Spontaneous absorption (D) Spontaneous emission
39. Hay's bridge  
(A) Is particularly suited for measurement of capacitance over a wide range of values  
(B) Is particularly suited for measurement of inductance having high Q value  
(C) Is suited for measurement of capacitance having high Q value  
(D) Is suited for measurement of inductance having low Q value
40. Meggar is an instrument for  
(A) Measuring current (B) Measuring voltage  
(C) Testing insulation (D) Measuring power
41. Resolution of a measuring instrument is defined as  
(A) Ratio of change of output signal to change in the input signal  
(B) Consistency or reproducibility of the measurement  
(C) Ability to reproduce the output in the same form as the input  
(D) The smallest measureable input change
42. Bioelectric potentials related to muscle activity constitute  
(A) Electromyogram (B) Electroencephalogram  
(C) Electrocardiogram (D) Electrooculograph
43. Which of the following variables cannot be measured directly by a CRO  
(A) Current (B) Voltage  
(C) Phase difference (D) Frequency

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

44. The reverse current in a diode is of the order of  
(A) kA (B) mA  
(C)  $\mu$ A (D) A
45. In an unregulated power supply, if the load current increases, the output voltage  
(A) Remains same (B) Decreases  
(C) Increases (D) None of the above
46. Which of the following are the main components of a tank circuit  
(A) R and L (B) L and C  
(C) R and C (D) None of the above
47. Which of the following configurations has the highest current gain?  
(A) Common base (B) Voltage follower  
(C) Common emitter (D) Common collector
48. Which of the following is a volatile memory device?  
(A) Hard disk (B) Floppy disk  
(C) Magnetic type (D) RAM
49. Commercial power supplies have voltage regulation  
(A) Of within 1% (B) Of 10%  
(C) Of 15% (D) Of 25%
50. In FM for a given frequency deviation, the modulation index varies  
(A) Inversely as the modulating frequency (B) Directly as the modulating frequency  
(C) Independent of the modulating frequency (D) None of the above
51. Quantizing noise occurs in  
(A) Time division multiplexing (B) PCM  
(C) PPM (D) Frequency division multiplexing
52. The scale of a voltmeter is uniform. Its type is  
(A) Moving iron (B) Induction  
(C) Moving coil permanent magnet (D) Moving coil dynamometer
53. A digital voltmeter has a read out range from 0 to 999 counts. If the full scale reading is 9.999V, the resolution is  
(A) 1 mV (B) 0.01 V  
(C) 1 V (D) 1  $\mu$ V

WRITTEN TEST FOR THE POST OF JR. TECHNICAL ASSISTANT (ELECTRONICS)—A

54. In input impedance of a CRO is about  
(A) 0 (B)  $10\Omega$   
(C)  $100\Omega$  (D)  $1M\Omega$
55. What is the range of a 3 1/2 digit, digital voltmeter?  
(A) 0 to 1999 (B) 0 to 1500  
(C) 0 to 999 (D) 0 to 19999
56. A dual trace oscilloscope usually offers two modes, chop and alternate. The alternate mode can be used for displaying:  
(A) Any two waveforms  
(B) Two waveforms of relatively high frequency  
(C) Two waveforms of relatively low frequency  
(D) One low frequency waveform and one high frequency waveform
57. The usage of electronic instruments is becoming more extensive because they have  
(A) A high sensitivity and reliability  
(B) A fast response and compatibility with digital computers  
(C) The capability to respond to signals from remote places  
(D) All of the above
58. Production of deep heat directly in the tissues of the body is achieved by  
(A) Bio telemetry (B) Diathermy  
(C) Defibrillator (D) Pacemaker
59. In modern electronic multimeters, a FET or MOSFET is preferred over BJT because  
(A) Its input resistance is high  
(B) Its input resistance is high and does not vary with change of range  
(C) Its input resistance is low  
(D) It is cheaper
60. The fastest A/D converter is  
(A) Flash type (B) Successive approximation type  
(C) Dual slope type (D) None of the above



**JR. TECH. ASST. (ELECTRONICS)-A-ANSWER KEY (07/07/2017)**

1	B	21	C	41	D
2	B	22	A	42	A
3	A	23	D	43	A
4	D	24	B	44	C
5	C	25	C	45	B
6	C	26	C	46	B
7	B	27	D	47	D
8	A	28	A	48	D
9	C	29	D	49	A
10	D	30	A	50	A
11	B	31	C	51	B
12	D	32	D	52	C
13	B	33	D	53	A
14	C	34	D	54	D
15	A	35	B	55	A
16	D	36	D	56	B
17	D	37	A	57	D
18	B	38	B	58	B
19	C	39	B	59	A
20	A	40	C	60	A